



Birzeit University  
Faculty of Engineering and Technology  
Department of Electrical and Computer Engineering

**Project**  
**Advanced Digital System Design**

Prepared by  
Name: Hasan Qarmash  
ID: 1210611

Supervised by  
Dr. Abdallatif Abuissa

## **Abstract**

The aim of this project to be familiar with Verilog HDL and Understanding the working mechanism of the counters, specifically the prime number system and the Fibonacci system

# Contents

<b>1</b>	<b>project course</b>	<b>1</b>
1.1	My way of thinking . . . . .	1
1.1.1	T-FlipFlop . . . . .	2
1.1.2	prime number UP . . . . .	2
1.2	Prime Down . . . . .	5
1.2.1	truth table prime Down . . . . .	6
1.2.2	Code prime down & Test bench . . . . .	6
1.3	Fibonacci number UP . . . . .	9
1.3.1	Truth table Fibonacci UP . . . . .	10
1.3.2	Code Fibonacci UP & Test bench . . . . .	10
1.3.3	Circuits and Summation SOP . . . . .	11
1.4	Fibonacci number Down . . . . .	12
1.4.1	Truth table Fibonacci Down . . . . .	13
1.4.2	Code Fibonacci Down & Test bench . . . . .	13
1.4.3	Circuits and Summation SOP . . . . .	14
1.5	All System . . . . .	15
1.5.1	type Mood . . . . .	15
1.5.2	Output System . . . . .	15
1.5.3	Code . . . . .	17
1.5.4	Test bench System . . . . .	17
1.6	Test Generator & System Analyzer & Verification . . . . .	20
<b>2</b>	<b>Conclusion</b>	<b>21</b>

## List of Figures

1	Plan project . . . . .	1
2	code T-FLIPFLOP . . . . .	2
3	Truth Table prime up counter . . . . .	2
4	code prime up . . . . .	3
5	code Test bench . . . . .	3
6	Result For K-map and Circuit For prime up counter . . . . .	4
7	SOP & characteristic equation For counter prime up . . . . .	5
8	run test bench result For counter prime up . . . . .	5
9	Truth Table prime down counter . . . . .	6
10	code prime down . . . . .	6
11	code Test bench . . . . .	7
12	SOP & characteristic equation For counter prime Down . . . . .	7
13	run test bench result For counter prime Down . . . . .	8
14	Result For K-map and Circuit For prime Down counter . . . . .	9
15	Truth Table Fibonacci UP counter . . . . .	10
16	code Fibonacci UP . . . . .	10
17	code Test bench . . . . .	11
18	Circuits and Summation SOP For Fibonacci UPcounter . . . . .	12
19	Truth Table Fibonacci Down counter . . . . .	13
20	code Fibonacci Down . . . . .	13
21	code Test bench . . . . .	14
22	Circuits and Summation SOP For Fibonacci DOWN counter . . . . .	15
23	code all system . . . . .	17
24	code Test bench for all system . . . . .	17
25	code Test bench for all system part two . . . . .	18
26	explain . . . . .	20

# 1 project course

In this project, we will build a structural circuit using T-Flip Flops and combination logic, that can count either Prime numbers or Fibonacci depends on a value of an input. Also, it can count them either up or down depends on the value of another input. The counter should count the first 11 numbers of any sequence Figure 1: Plan project as shown in Figure 1 , in two different stages by using Aldec Active-HDL student Edition to write Verilog codes,

 


Figure 1: Plan project

- prime number UP:2,3,5,7,11,13,17,19,23,29,31
- prime number Down:31,29,23,19,17,13,11,7,5,3,2
- Fibonacci number UP:0,1,1,2,3,5,8,13,21,34,55
- Fibonacci number Down:55,34,21,13,8,5,3,2,1,1,0

## 1.1 My way of thinking

I divided the counters into four types in order to facilitate the design process, especially since in Fibonacci system there is 6-bit and with the entry of ascending and descending it becomes 7 and with the entry the system determines if it is Fibonacci or prime it becomes I have 8 and this is outside the framework of my ability to represent. so The types is:

**prime number UP**

**prime number Down**

**Fibonacci number UP**

**Fibonacci number Down**

### 1.1.1 T-FlipFlop

A T-flip flop, also known as a toggle flip flop, is a type of sequential logic circuit that can store and toggle its state based on the input signal. It has one input, denoted as T, and two outputs: Q (the current state) and Q' (the complement of the current state). The behavior of a T-flip flop is determined by its characteristic table, which specifies the output states based on the current input and the previous state

**Hint:** The T-flip flop active high That mean when reset =1 result Q=0;

```

134 module T_ff(t,clk,reset,q);
135
136 input t,clk,reset;
137 output q;
138 reg q;
139 always @(posedge clk or posedge reset) begin
140 if(reset) begin
141 q=1'b0;
142 end
143 else
144 begin
145 q<=q^t;
146 end
147 end
148 endmodule
149

```

Figure 2: code T-FLIPFLOP

### 1.1.2 prime number UP

A prime number is a natural number greater than 1 that cannot be divided evenly by any other natural number except for 1 and itself. In other words, a prime number has exactly two distinct positive divisors: 1 and the number itself.

Here are the first 11 prime numbers:

2, 3, 5, 7, 11, 13, 17, 19, 23, 29, 31,

// Truth table for prime number UP											T-Flip Flop				
//Present state					Next state						T4	T3	T2	T1	T0
// Q4	Q3	Q2	Q1	Q0	Q4	Q3	Q2	Q1	Q0						
// 0	0	0	1	0	0	0	0	1	1	0	0	0	0	1	
// 0	0	0	1	1	0	0	1	0	1	0	0	1	1	0	
// 0	0	1	0	1	0	0	1	1	1	0	0	0	1	0	
// 0	0	1	1	1	0	1	0	1	1	0	1	1	0	0	
// 0	1	0	1	1	0	1	1	0	1	0	0	1	1	0	
// 0	1	1	0	1	1	0	0	0	1	1	1	1	0	0	
// 1	0	0	0	1	1	1	0	0	1	0	0	0	1	0	
// 1	0	0	1	1	1	1	0	1	1	0	0	1	0	0	
// 1	0	1	1	1	1	1	1	0	1	0	1	0	1	0	
// 1	1	1	0	1	1	1	1	1	1	0	0	0	1	0	
// 1	1	1	1	1	1	0	0	0	1	0	1	1	0	1	

Figure 3: Truth Table prime up counter

```

157
158 module PrimeUP(clk,Q,reset);
159     input clk,reset;
160     output [4:0]Q;
161     wire [4:0]D;
162     assign D[0]=~Q[0]|(Q[3] & Q[2] & Q[1]);
163     assign D[1]=(~Q[3]& ~Q[1])|(Q[4] & ~Q[1]) |(~Q[4] & ~Q[2] & Q[0])|(Q[4] & ~Q[3] & Q[2]);
164     assign D[2]=(~Q[4]& Q[3])|(Q[3] & Q[1]) |(~Q[4] & Q[1] & Q[0]) | (~Q[2] & Q[1] & Q[0]);
165     assign D[3]=(Q[2]& Q[1])|(~Q[4] & Q[3] & ~Q[1]);
166     assign D[4]=(~Q[4] & Q[3] & ~Q[1])|(Q[3] & Q[2] & Q[1]);
167
168     T_ff U0(D[0],clk,reset,Q[0]);
169     T_ff U1(D[1],clk,reset,Q[1]);
170     T_ff U2(D[2],clk,reset,Q[2]);
171     T_ff U3(D[3],clk,reset,Q[3]);
172     T_ff U4(D[4],clk,reset,Q[4]);
173
174 endmodule
175

```

Figure 4: code prime up

```

module testPrimeNumberUP;
    reg clk,reset;
    wire [4:0]Q;
    PrimeUP R0(clk,Q,reset);
    initial
        begin
            reset = 1'b1;clk=1;
            $monitor("%b%b%b%b%b",Q[4],Q[3],Q[2],Q[1],Q[0]);
            #10ns reset = 0;
            repeat (53)
                #10ns clk = ~clk;
            end
        end
endmodule

```

Figure 5: code Test bench

when i do k-map the result is as follows

Hint: I have created k-map and circuit in a dedicated site, so if you want to check the site, press the number [1]

$y = T$

$A = Q[4]$


$B = Q[3]$

$C = Q[2]$


$D = Q[1]$

$E = Q[0]$


for This picture

 


(a) Circuit T0 in prime up

 

(b) Circuit T1 in prime up

 

(c) Circuit T2 in prime up

 

(d) Circuit T3 in prime up

Figure 6: Result For K-map and Circuit For prime up counter



```

16 //T0={2,31}
17 //T1={3,5,11,17,23,29}
18 //T2={3,7,11,13,19,31}
19 //T3={7,13,23,31}
20 //T4={13,31}
21
22 //T0=Q0' +Q3Q2Q1
23 //T1=Q3'Q1'+Q4Q1'+Q4'Q2'Q0+Q4Q3'Q2
24 //T2=Q4'Q3+Q3Q1+Q4'Q1Q0+Q2'Q1Q0
25 //T3=Q2Q1+Q4'Q3Q1'
26 //T4=Q4'Q3Q1'+Q3Q2Q1
27

```

Figure 7: SOP & characteristic equation For counter prime up

```

◦ # KERNEL: 00010
◦ # KERNEL: 00011
◦ # KERNEL: 00101
◦ # KERNEL: 00111
◦ # KERNEL: 01011
◦ # KERNEL: 01101
◦ # KERNEL: 10001
◦ # KERNEL: 10011
◦ # KERNEL: 10111
◦ # KERNEL: 11101
◦ # KERNEL: 11111
◦ # KERNEL: 00010

```

Figure 8: run test bench result For counter prime up

## 1.2 Prime Down

Here are the first 11 prime numbers:

31,29,23,19,17,13,11,7,5,3,2

### 1.2.1 truth table prime Down

// Truth table for prime number Down											T-Flip Flop				
//Present state						Next state									
//	Q4	Q3	Q2	Q1	Q0	Q4	Q3	Q2	Q1	Q0	T4	T3	T2	T1	T0
//	0	0	0	1	0	1	1	1	1	1	1	1	1	0	1
//	0	0	0	1	1	0	0	0	1	0	0	0	0	0	1
//	0	0	1	0	1	0	0	0	1	1	0	0	1	1	0
//	0	0	1	1	1	0	0	1	0	1	0	0	0	1	0
//	0	1	0	1	1	0	0	1	1	1	0	1	1	0	0
//	0	1	1	0	1	0	1	0	1	1	0	0	1	1	0
//	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0
//	1	0	0	1	1	1	0	0	0	1	0	0	0	1	0
//	1	0	1	1	1	1	0	0	1	1	0	0	1	0	0
//	1	1	1	0	1	1	0	1	1	1	0	1	0	1	0
//	1	1	1	1	1	1	1	1	0	1	0	0	0	1	0

Figure 9: Truth Table prime down counter

### 1.2.2 Code prime down & Test bench

```

185 module primeDwon(clk,Q,reset);
186 input clk,reset;
187 output [4:0]Q;
188 wire [4:0]D;
189
190 assign D[0]=(~Q[4] & ~Q[3] & ~Q[2]);
191 assign D[1]=(~Q[4] & Q[2]) |(Q[3] & Q[2]) |(Q[4] & ~Q[2] & Q[1]);
192 assign D[2]=(~Q[0])|(~Q[4]& ~Q[1])|(~Q[2] & ~Q[1]) |(~Q[4] & Q[3]) | (Q[4] & ~Q[3] & Q[2] & Q[1]);
193 assign D[3]=(~Q[0])|(~Q[2]& ~Q[1])|(Q[3]& ~Q[2])|(Q[4] & Q[3] & ~Q[1]);
194 assign D[4]=(~Q[0])|(~Q[2] & ~Q[1]);
195
196
197 T_ff U0(D[0],clk,reset,Q[0]);
198 T_ff U1(D[1],clk,reset,Q[1]);
199 T_ff U2(D[2],clk,reset,Q[2]);
200 T_ff U3(D[3],clk,reset,Q[3]);
201 T_ff U4(D[4],clk,reset,Q[4]);
202 endmodule

```

Figure 10: code prime down

```

204 module testPrimeNumberDwon;
205     reg clk,reset;
206     wire [4:0]Q;
207     primeDwon R1(clk,Q,reset);
208     initial
209     begin
210         reset = 1'b1;clk=1;
211         $monitor("%b%b%b%b%b",Q[4],Q[3],Q[2],Q[1],Q[0]);
212         #10ns reset = 0;
213         repeat (53)
214             #10ns clk = ~clk;
215         end
216     endmodule
217

```

Figure 11: code Test bench

```

62 //T0={2,3}
63 //T1={5,7,13,19,29,31}
64 //T2={2,5,11,13,17,23}
65 //T3={2,11,17,29}
66 //T4={2,17}
67
68 //T0=Q4'Q3'Q2'
69 //T1= Q4'Q2+Q3Q2+Q4Q2'Q1
70 //T2= Q0'+Q4'Q1'+Q2'Q1'+Q3'Q3+Q4Q3'Q2Q1
71 //T3=Q0'+Q2'Q1'+Q3Q2'+Q4Q3Q1'
72 //T4=Q0'+Q2'Q1'
73
74

```

Figure 12: SOP & characteristic equation For counter prime Down

```

◦ # KERNEL: 11111
◦ # KERNEL: 11101
◦ # KERNEL: 10111
◦ # KERNEL: 10011
◦ # KERNEL: 10001
◦ # KERNEL: 01101
◦ # KERNEL: 01011
◦ # KERNEL: 00111
◦ # KERNEL: 00101
◦ # KERNEL: 00011
◦ # KERNEL: 00010
◦ # KERNEL: 11111

```

Figure 13: run test bench result For counter prime Down

**Hint:**I have created k-map and circuit in a dedicated site, so if you want to check the site, press the number [1]

y=T

A= Q[4]


B=Q[3]

C= Q[2]


D= Q[1]

E= Q[0]


for This picture

 


(a) Circuit T1 in prime down

 

(b) Circuit T2 in prime down

 

(c) Circuit T3 in prime down

 

(d) Circuit T4 in prime down

Figure 14: Result For K-map and Circuit For prime Down counter

### 1.3 Fibonacci number UP

Fibonacci numbers are a sequence of numbers in which each number is the sum of the two preceding ones. The sequence starts with 0 and 1, and the subsequent numbers are generated by adding the previous two numbers together.

Here are the first few Fibonacci numbers:

0, 1, 1, 2, 3, 5, 8, 13, 21, 34, 55, 89, 144, ...

The Fibonacci sequence can be defined recursively by the following formula:

$$F(n) = F(n - 1) + F(n - 2)$$

where  $F(0) = 0$  and  $F(1) = 1$ .

Fibonacci numbers have many interesting properties and can be found in various areas of mathematics and nature. They often appear in patterns in biological systems,

art, and even financial markets.

### 1.3.1 Truth table Fibonacci UP

77	// Truth table for Fibb number UP																			
78	//Present state							Next state							T-Flip Flop					
79	//	Q5	Q4	Q3	Q2	Q1	Q0	Q5	Q4	Q3	Q2	Q1	Q0	T5	T4	T3	T2	T1	T0	
80	//	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	s0
81	//	0	0	0	0	0	1	0	0	0	0	1	0	0	0	0	0	1	1	s1
82	//	0	0	0	0	0	1	0	0	0	0	1	0	0	0	0	0	1	1	sR ----- Error
83	//	0	0	0	0	1	0	0	0	0	0	1	1	0	0	0	0	0	1	s2
84	//	0	0	0	0	1	1	0	0	0	1	0	1	0	0	0	1	1	0	s3
85	//	0	0	0	1	0	1	0	0	1	0	0	0	0	0	1	1	0	1	s5
86	//	0	0	1	0	0	0	0	0	1	1	0	1	0	0	0	1	0	1	s8
87	//	0	0	1	1	0	1	0	1	0	1	0	1	0	1	1	0	0	0	s13
88	//	0	1	0	1	0	1	1	0	0	0	1	0	1	1	0	1	1	1	s21
89	//	1	0	0	0	1	0	1	1	0	1	1	1	0	1	0	1	0	1	s34
90	//	1	1	0	1	1	1	0	0	0	0	0	0	1	1	0	1	1	1	s55
91																				

Figure 15: Truth Table Fibonacci UP counter

### 1.3.2 Code Fibonacci UP & Test bench

```

282 module FibbUP(clk,Q,reset);
283 input clk,reset;
284 output [5:0]Q;
285 wire [5:0]D;
286     assign D[0]=~Q[0]|(Q[4])|(~Q[3] & ~Q[1]);
287     assign D[1]=(Q[4])|(~Q[2]& Q[0]);
288     assign D[2]=(Q[5])|(Q[1]& Q[0])|(~Q[3] & Q[2]) | (Q[3] & ~Q[2]);
289     assign D[3]=(~Q[4] & Q[2]);
290     assign D[4]=(Q[4]) | (Q[5]) | (Q[3] & Q[0]);
291     assign D[5]=Q[4];
292     T_ff U0(D[0],clk,reset,Q[0]);
293     T_ff U1(D[1],clk,reset,Q[1]);
294     T_ff U2(D[2],clk,reset,Q[2]);
295     T_ff U3(D[3],clk,reset,Q[3]);
296     T_ff U4(D[4],clk,reset,Q[4]);
297     T_ff U5(D[5],clk,reset,Q[5]);
298 endmodule

```

Figure 16: code Fibonacci UP

```

300 module testFibbUP;
301     reg clk,reset;
302     wire [5:0]Q;
303     FibbUP U(clk,Q,reset);
304     initial
305     begin
306         reset = 1'b1;clk=1;
307         $monitor("%b%b%b%b%b%b",Q[5],Q[4],Q[3],Q[2],Q[1],Q[0]);
308         #10ns reset = 0;
309         repeat (100)
310             #10ns clk = ~clk;
311         end
312     endmodule
313

```

Figure 17: code Test bench

### 1.3.3 Circuits and Summation SOP

I did not photograph all the circuits because they are simple with the caveat on the same note that I wrote earlier which was I have created k-map and circuit in a dedicated site, so if you want to check the site, press the number [1]

**Hint:I considered case 1-1 non-existent in Fibonacci Consecutive excuse me**

```

92 //T0={0,1,2,5,8,21,34,55}
93 //T1={1,3,21,55}
94 //T2={3,5,8,21,34,55}
95 //T3={5,13}
96 //T4={13,21,34,55}
97 //T5={21,55}
98
99 //T0=Q0'+Q3'Q2
100 //T1=Q4+Q1Q0
101 //T2=Q5+Q1Q0+Q3'Q2+Q3Q2'
102 //T3=Q4'Q2
103 //T4=Q4+Q5+Q3Q0
104 //T5=Q4

```


(a) SOP & characteristic equation

```


◦ # KERNEL: 000000
◦ # KERNEL: 000001
◦ # KERNEL: 000010
◦ # KERNEL: 000011
◦ # KERNEL: 000101
◦ # KERNEL: 001000
◦ # KERNEL: 001101
◦ # KERNEL: 010101
◦ # KERNEL: 100010
◦ # KERNEL: 110111
◦ # KERNEL: 000000

```

(b) Result Of RUN testbench

 

(c) Circuit T0 in Fibonacci UP

 

(d) Circuit T1 in Fibonacci UP

Figure 18: Circuits and Summation SOP For Fibonacci UPcounter

## 1.4 Fibonacci number Down

Here are the first 11 Fibonacci number Down:

55,34,21,13,8,5,3,2,1,1,0



### 1.4.1 Truth table Fibonacci Down

// Truth table for Fibb number Dwon												T-Flip Flop						
//Present state						Next state						T5	T4	T3	T2	T1	T0	
// Q5	Q4	Q3	Q2	Q1	Q0	Q5	Q4	Q3	Q2	Q1	Q0							
// 0	0	0	0	0	0	1	1	0	1	1	1	1	1	0	1	1	1	s0
// 0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	1	s1
// 0	0	0	0	0	1	0	0	0	0	1	1	0	0	0	1	1	1	sR ---
// 0	0	0	0	1	0	0	0	0	0	0	1	0	0	0	0	1	1	s2
// 0	0	0	0	1	1	0	0	0	0	1	0	0	0	0	0	0	1	s3
// 0	0	0	1	0	1	0	0	0	0	1	1	0	0	0	1	1	0	s5
// 0	0	1	0	0	0	0	0	0	1	0	1	0	0	1	1	0	1	s8
// 0	0	1	1	0	1	0	0	1	0	0	0	0	0	0	1	0	1	s13
// 0	1	0	1	0	1	0	0	1	1	0	1	0	1	1	0	0	0	s21
// 1	0	0	0	1	0	0	1	0	1	0	1	1	1	0	1	1	1	s34
// 1	1	0	1	1	1	1	0	0	0	1	0	0	1	0	1	0	1	s55

Figure 19: Truth Table Fibonacci Down counter

### 1.4.2 Code Fibonacci Down & Test bench

```

303 module FibbDown(clk,Q,reset);
304 input clk,reset;
305 output [5:0]Q;
306 wire [5:0]D;
307 assign D[0]=~Q[2]|| Q[0] | Q[3];
308 assign D[1]=(~Q[3] & ~Q[0])|(~Q[4]& ~Q[3] & Q[2]);
309 assign D[2]=(Q[5])|(~Q[1]& ~Q[0])|(~Q[3] & Q[2]);
310 assign D[3]=(Q[3] & ~Q[2])|(~Q[5] & Q[4]);
311 assign D[4]=(Q[4]) | (Q[5]) | (~Q[3] & ~Q[1] & ~Q[0]);
312 assign D[5]=(Q[5] & ~Q[4]) | (~Q[3] & ~Q[1] & ~Q[0]);
313 T_ff U0(D[0],clk,reset,Q[0]);
314 T_ff U1(D[1],clk,reset,Q[1]);
315 T_ff U2(D[2],clk,reset,Q[2]);
316 T_ff U3(D[3],clk,reset,Q[3]);
317 T_ff U4(D[4],clk,reset,Q[4]);
318 T_ff U5(D[5],clk,reset,Q[5]);
319 endmodule

```

Figure 20: code Fibonacci Down

```

module testFibbDown;
    reg clk,reset;
    wire [5:0]Q;
    FibbDown U(clk,Q,reset);
    initial
        begin
            reset = 1'b1;clk=1;
            $monitor("%b%b%b%b%b%b",Q[5],Q[4],Q[3],Q[2],Q[1],Q[0]);
            #10ns reset = 0;
            repeat (100)
                #10ns clk = ~clk;
            end
        endmodule

```

Figure 21: code Test bench

### 1.4.3 Circuits and Summation SOP

I did not photograph all the circuits because they are simple with the caveat on the same note that I wrote earlier which was I have created k-map and circuit in a dedicated site, so if you want to check the site, press the number [1]

**Hint:**I considered case 1-1 non-existent in Fibonacci Consecutive excuse me

```

109 //T0={0,1,2,3,8,13,34,55}
110 //T1={0,2,5,34}
111 //T2={0,5,8,13,34,55}
112 //T3={8,21}
113 //T4={0,21,34,55}
114 //T5={0,34}
115
116 //T0=Q2'+Q0+Q3
117 //T1=Q3'Q0'+Q4'Q2'Q3'
118 //T3=Q3Q2'+Q5'Q4
119 //T4=Q4+Q5+Q3'Q2'Q0'
120 //T5=Q5Q4'+Q3'Q2'Q0'

```

(a) SOP & characteristic equation

```

◦ # KERNEL: 110111
◦ # KERNEL: 100010
◦ # KERNEL: 010101
◦ # KERNEL: 001000
◦ # KERNEL: 000101
◦ # KERNEL: 000010
◦ # KERNEL: 000001
◦ # KERNEL: 000000
◦ # KERNEL: 110111
◦ # KERNEL: 100010
◦ # KERNEL: 010101
◦ # KERNEL: 001000
◦ # KERNEL: 000101

```

(b) Result Of RUN testbench

Map															
ABC	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF
ABC	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
ABC	1	x	x	x	x	x	x	1	x	x	x	x	x	x	x
ABC	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
ABC	x	x	x	x	x	x	x	0	x	x	x	x	x	x	x
ABC	x	x	x	x	x	x	x	1	x	x	x	x	x	x	x
ABC	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
ABC	x	x	x	x	x	x	x	x	x	x	x	x	x	x	x
ABC	x	x	x	x	x	x	x	1	x	x	x	x	x	x	x

Map Layout															
ABC	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF
ABC	0	1	3	2	4	5	7	6							
ABC	8	9	11	10	12	13	15	14							
ABC	24	25	27	26	28	29	31	30							
ABC	16	17	19	18	20	21	23	22							
ABC	32	33	35	34	36	37	39	38							
ABC	40	41	43	42	44	45	47	46							
ABC	56	57	59	58	60	61	63	62							
ABC	48	49	51	50	52	53	55	54							

Groups															
(0,1,2,3,8,9,10,11,16,17,18,19,24,25,26,27,32,33,34,35,40,41,42,43,48,49,50,51,56,57,58,59)															D
(2,3,6,7,10,11,14,15,18,19,22,23,26,27,30,31,34,35,38,39,42,43,46,47,50,51,54,55,58,59,62,63)															E
(8,9,10,11,12,13,14,15,24,25,26,27,28,29,30,31,40,41,42,43,44,45,46,47,56,57,58,59,60,61,62,63)															C

(c) Circuit T0 in Fibonacci UP

SUM of PRODUCTS															
ABC	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF
ABC	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
ABC	0	1	3	2	4	5	7	6							
ABC	8	9	11	10	12	13	15	14							
ABC	24	25	27	26	28	29	31	30							
ABC	16	17	19	18	20	21	23	22							
ABC	32	33	35	34	36	37	39	38							
ABC	40	41	43	42	44	45	47	46							
ABC	56	57	59	58	60	61	63	62							
ABC	48	49	51	50	52	53	55	54							

Map Layout															
ABC	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF	DEF
ABC	0	1	3	2	4	5	7	6							
ABC	8	9	11	10	12	13	15	14							
ABC	24	25	27	26	28	29	31	30							
ABC	16	17	19	18	20	21	23	22							
ABC	32	33	35	34	36	37	39	38							
ABC	40	41	43	42	44	45	47	46							
ABC	56	57	59	58	60	61	63	62							
ABC	48	49	51	50	52	53	55	54							

Groups															
(0,2,4,6,16,18,20,22,24,26,28,48,50,52,54)															CF
(4,5,6,7,26,27,38,39)															BCD

y = CF + BCD

(d) Circuit T1 in Fibonacci down

Figure 22: Circuits and Summation SOP For Fibonacci DOWN counter

## 1.5 All System

This system collects the four counters and makes the selection based on the input  
**prime number UP**

**prime number Down**

**Fibonacci number UP**

**Fibonacci number Down**

### 1.5.1 type Mood

if Mood=2'b00 Then **prime number Down**

if Mood=2'b01 Then **prime number UP**

if Mood=2'b10 Then **Fibonacci number UP**

if Mood=2'b11 Then **Fibonacci number Down**

### 1.5.2 Output System

I made four outputs and they are as follows

**outputPrimeUP**

**outputPrimeDwon**

**outputFibbUP**

**outputFibbDown**

For example if it is Mood =2'b00 it means that the counter has build is prime down between other counter is reset(equal zero)

### 1.5.3 Code

```
207 module SystemAll(clk,outputPrimeUP,outputPrimeDwon,outputFibbUP,outputFibbDown,Mood);
208   input  clk;
209   input  [1:0]Mood;
210   output [4:0]outputPrimeUP,outputPrimeDwon;
211   output [5:0]outputFibbUP,outputFibbDown;
212   wire [3:0]yourChoice;
213   //prime down
214   assign yourChoice[0]= (Mood==2'b00)?1'b0:1'b1;
215   //prime UP
216   assign yourChoice[1]= (Mood==2'b01)?1'b0:1'b1;
217   //Fibonacci Down
218   assign yourChoice[2]= (Mood==2'b10)?1'b0:1'b1;
219   //Fibonacci UP
220   assign yourChoice[3]= (Mood==2'b11)?1'b0:1'b1;
221   PrimeUP  R0(clk,outputPrimeUP,yourChoice[0]) ;
222   primeDwon R1(clk,outputPrimeDwon,yourChoice[1]);
223   FibbUP    R2(clk,outputFibbUP,yourChoice[2]);
224   FibbDown  R3(clk,outputFibbDown,yourChoice[3]);
225 endmodule
226
```

Figure 23: code all system

### 1.5.4 Test bench System

```
227 module testAllSystem;
228   reg clk;
229   reg [1:0]Mood;
230   wire [4:0]outputPrimeUP,outputPrimeDwon;
231   wire [5:0]outputFibbUP,outputFibbDown;
232   SystemAll S(clk,outputPrimeUP,outputPrimeDwon,outputFibbUP,outputFibbDown,Mood);
233   initial
234     begin
235       Mood=2'b00;
236       clk=1;
237       $monitor("Up prime:%b%b%b%b",outputPrimeUP[4],outputPrimeUP[3],outputPrimeUP[2],outputPrimeUP[1],outputPrimeUP[0]);
238       $monitor("Down prime:%b%b%b%b",outputPrimeDwon[4],outputPrimeDwon[3],outputPrimeDwon[2],outputPrimeDwon[1],outputPrimeDwon[0]);
239       $monitor("up Fibb:%b%b%b%b",outputFibbUP[5],outputFibbUP[4],outputFibbUP[3],outputFibbUP[2],outputFibbUP[1],outputFibbUP[0]);
240       $monitor("Down Fibb:%b%b%b%b",outputFibbDown[5],outputFibbDown[4],outputFibbDown[3],outputFibbDown[2],outputFibbDown[1],outputFibbDown[0]);
241       repeat(60)
242         begin
243           #10ns clk=~clk;
244         end
245       #10ns Mood=2'b01;
246       repeat(60)
247         begin
248           #10ns clk=~clk;
249         end
250       #10ns Mood=2'b10;
```

Figure 24: code Test bench for all system

```

241
242
243
244
245
246
247
248
249
250
251
252
253
254
255
256
257
258
259
260
261
endmodule

repeat(60)
begin
#10ns clk=~clk;
end
#10ns Mood=2'b01;
repeat(60)
begin
#10ns clk=~clk;
end
#10ns Mood=2'b10;
repeat(60)
begin
#10ns clk=~clk;
end
#10ns Mood=2'b11;
repeat(60)
begin
#10ns clk=~clk;
end
end

```

Figure 25: code Test bench for all system part two

```

run # Simulation has been initialized run KERNEL: Down prime:xxxxxx
KERNEL: Up prime:00000
KERNEL: up Fibb:000000
KERNEL: Down Fibb:000000
KERNEL: Down prime:00000
KERNEL: Up prime:00011
KERNEL: Up prime:00101
KERNEL: Up prime:00111
KERNEL: Up prime:01011
KERNEL: Up prime:01101
KERNEL: Up prime:10001
KERNEL: Up prime:10011
KERNEL: Up prime:00000
KERNEL: Down prime:11101
KERNEL: Down prime:10111
KERNEL: Down prime:10011
KERNEL: Down prime:10001
KERNEL: Down prime:01101
KERNEL: Down prime:01011
KERNEL: Down prime:00111
KERNEL: Down prime:00101
KERNEL: Down prime:00000
KERNEL: up Fibb:000001
KERNEL: up Fibb:000010
KERNEL: up Fibb:000011
KERNEL: up Fibb:000101
KERNEL: up Fibb:001000
KERNEL: up Fibb:001101
KERNEL: up Fibb:010101
KERNEL: up Fibb:000000
KERNEL: Down Fibb:110111
KERNEL: Down Fibb:100010
KERNEL: Down Fibb:010101
KERNEL: Down Fibb:001000
KERNEL: Down Fibb:000101

```

KERNEL: Down Fibb:000010  
KERNEL: Down Fibb:000001  
KERNEL: Down Fibb:000000

# KERNEL: Simulation has finished. There are no more test vectors to simulate

**We note that if we were, for example, in state up Down prime:00000 and came after clk and Mood become 2'b10 then this makes Next State equal up Fibb:000001.**

## 1.6 Test Generator & System Analyzer & Verification

This section is one of the most important sections, and I would have liked to do it, but time did not help me, and I will only explain it

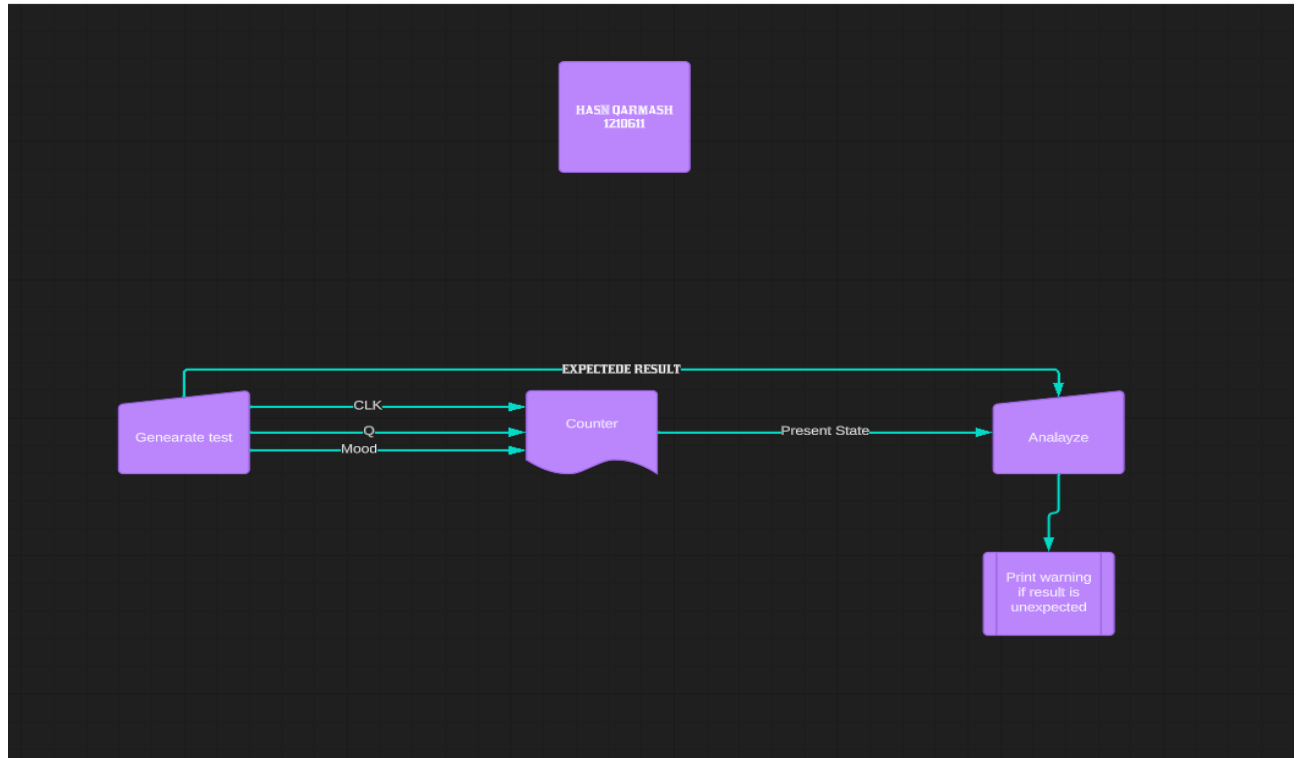


Figure 26: explain

A test generator code in Verilog is a piece of code that is designed to provide test stimuli or inputs in order to test a design or module. The design under test (DUT) inputs are subjected to a set of instructions or patterns that are used to check the functioning of the DUT or to trigger certain test cases.

A test generator code's main function is to offer a methodical, automated mechanism to create input patterns so that the DUT is thoroughly tested. By putting the design through multiple test situations, it helps to confirm its accuracy and resilience.



## 2 Conclusion

In this project, we encountered a lot of obstacles, some of which we solved and others not, as one of these problems was the number of inputs 8, and this number I cannot deal with, especially since I chose the k-map method, so I divided the counters into four, and this makes it possible for me to do k-map and then complete the rest. The steps in the design, and I encountered another problem, which is that while I was doing the testBench process, the results that appeared were illogical, which made me repeat some steps in the design, and this consumed a lot of time, while the problem was not writing testBench correctly, one of the problems also, which is when I type code "all system" is not able to determine which outputs I can start, especially since some of the counters contain 5-bit and some of them contain 6-bit. The solution was to make four outputs for each counter, and in the event that one of them works, the value of the remainder will be zero. One of the problems that I could not solve is the Fibonacci sequence 0 - 1 - 1, which is how to make it repeat the same number twice. I thought a lot and searched for you, I could not find any results.

by the end of this The report My understanding of counters has deepened much more as I had a weakness in this subject and I reviewed the digital systems course, I hope you have been pleased while reading the report.

**With Best Wishes:)** .

## References

- [1] *K-map solver*. URL: <http://www.32x8.com/var6.html>.